

Phys 2212


Question 1:

A negatively charged oil drop is suspended in the air using an electric field. The direction of the electric field must be

- (a) From left to right
- (b) from right to left
- (c) upward
- (d) downward


Question 2:

Following diagrams show four different current (I) vs voltage (V) graphs. Which of the following graphs represents an ohmic resistor?

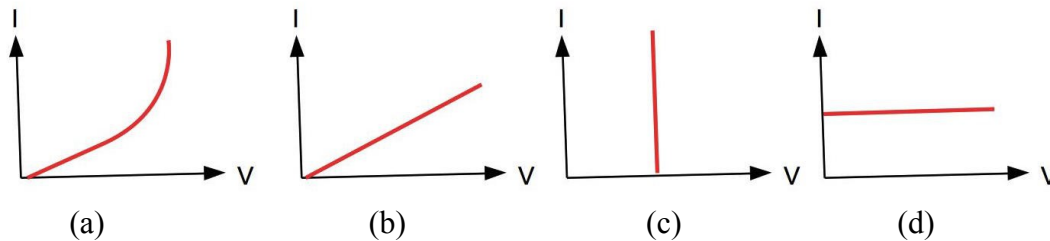

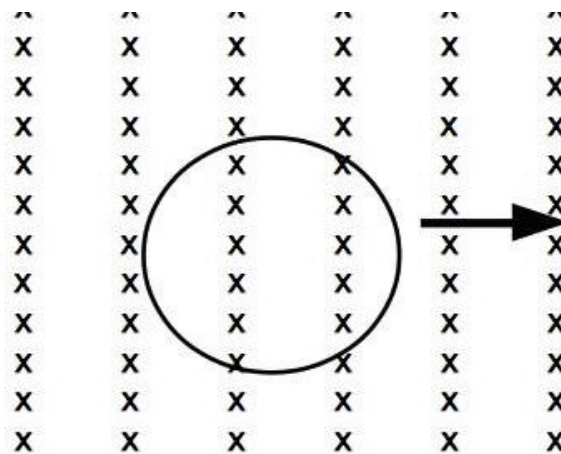Question 3:

A wire loop is moving in a uniform magnetic field at a constant speed as shown in the following diagram. The arrow shows the direction of the motion.




The motion does not induce any current in the loop. A possible reason could be

- (a) The loop is not moving at an acceleration
- (b) The motion of the loop is not in the direction of the magnetic field
- (c) There is no change in the magnetic flux in the loop
- (d) The loop is too small

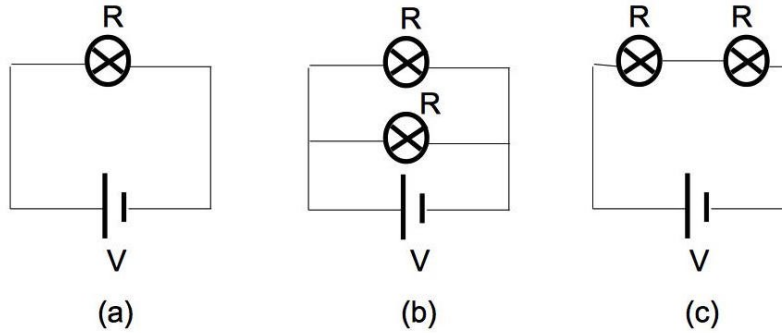Question 4:

Which following circuits produces the most light output? Assume that the light output is proportional to the total power output of the circuit. The bulbs are identical.




- (a) circuit (a)
- (b) circuit (b)
- (c) circuit (c)
- (d) same light output in all three circuits

Question 5:

In a thunderstorm which of the following actions would be the safest?

- (a) seek protection under a tree
- (b) stay at the top of a hill
- (c) stay inside your car
- (d) stay in an open space

Question 6:

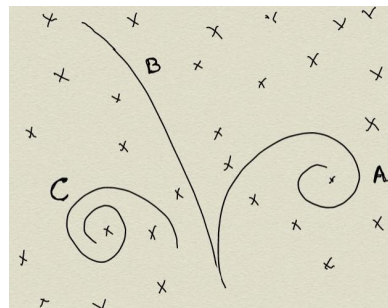

The above picture shows three charged particle tracks in a bubble chamber. The chamber is placed in a uniform magnetic field which is pointed into the plane of the paper. Choose the correct statement from the followings.

- (a) A represents a negatively charged particle
- (b) B and C represent negatively charged particles
- (c) C represents a negatively charged particle
- (d) A and C represent negatively charged particles


Question 7:

A series RCL circuit consists of a resistor, a capacitor and an inductor connected in series with $R=20\Omega$, $C=100\mu\text{F}$ and $L=120\text{mH}$. The capacitor and the inductor of an RCL circuit needs to be replaced with a different capacitor and an inductor to double the resonance frequency. Which of the followings will be most suitable capacitor-inductor combination to double the resonance frequency?

- (a) $C=50\mu\text{F}$, $L=60\text{mH}$
- (b) $C=200\mu\text{F}$, $L=30\text{mH}$
- (c) $C=50\mu\text{F}$, $L=240\text{mH}$
- (d) $C=200\mu\text{F}$, $L=240\text{mH}$

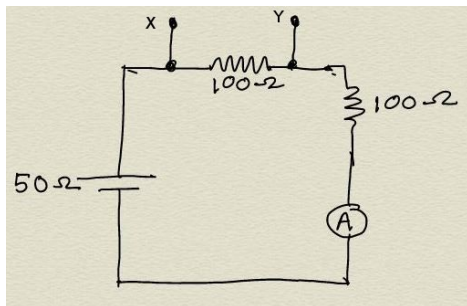Question 8:

The voltage drop across XY is measured using a voltmeter with a finite internal resistance. The internal resistance of the ammeter is negligible. When the voltmeter is connected across XY



- (a) the voltage across XY and the current in the ammeter decreases
- (b) the voltage across XY increases but the current in the ammeter decreases
- (c) the voltage across XY and the current in the ammeter increases
- (d) the voltage across XY decreases but the current in the ammeter increases

Question 9:


The electrostatic force between two point charges is 2N. If the distance between the charges is doubled, what will be the force between the two charges?

- (a) 0.5N
- (b) 1N
- (c) 2N
- (d) 4N

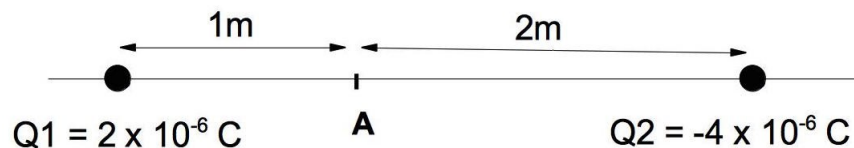Question 10:


Find the potential at point A due to the two point charges shown in the following diagram.

$$\left(k = \frac{1}{4\pi\epsilon_0} = 9 \times 10^9 \text{ N.m}^2/\text{C}^2\right)$$



- (a) 0V
- (b) 2000V
- (c) 36,000V
- (d) 20,000V

Question 11:

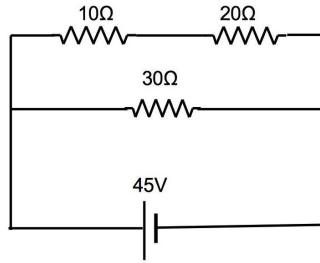

Find the current in the 30Ω resistor. Ignore the internal resistance of the battery.

- (a) 0.5A
- (b) 1.0A
- (c) 1.5A
- (d) 2.0A

Question 12:

Magnetic flux through a 100 turn coil is given by $\Phi_M = (12\text{V.s})\cos(8t)$. “t” is the time in seconds.

Find the maximum induced potential difference across the coil.

- (a) 1200V
- (b) 800V
- (c) 9600V
- (d) 150V