## Additional Homework Exercises

## Section 5: First Order Equations Models and Applications

(1) An RC-series circuit has resistance  $R_0$  and capacitance  $C_0$ . A constant electromotive force of  $E_0$  volts is applied. If the initial charge on the capacitor q(0) = 0, find the charge q(t) on the capacitor at time t. Show that the long time charge on the capacitor is the product  $E_0C_0$ .

(2) An LR-series circuit has inductance 0.5 h, resistance 10 ohms, and an applied force of  $0.1e^{-t}$  volts. If the initial current i(0) = 1A, find the current i(t).

(3) A 400 gallon tank contains water into which 10 lbs of salt is dissolved. Salt water containing 3 lbs of salt per gallon is being pumped in at a rate of 4 gallons per minute, and the well mixed solution is being pumped out at the same rate. Let A(t) be the number of lbs of salt in the tank at time t in minutes. Derive the initial value problem governing A(t). Solve this IVP for A.

(4) Suppose the solution in problem (3) is being pumped out at the rate of 5 gallons per minute. Keeping everything else the same as in problem (3), derive the IVP governing A under this new condition. Solve this IVP for A. What is the largest time value for which your solution is physically feasible?

(5) An LR-series circuit has constant inductance and resistance  $L_0$  and  $R_0$ , respectively. A constant electromotive force of  $E_0$  is applied. Find the current i(t) if  $i(0) = i_0$ . Show that for any initial current, the long time current in the circuit is  $E_0/R_0$ .

(6) We know that a quantity P that satisfies  $\frac{dP}{dt} = P$  experiences exponential growth. The equation  $\frac{dP}{dt} = P^{1+\epsilon}$ , for  $\epsilon > 0$ , is referred to as a *doomsday equation*. Solve the following IVP.

$$\frac{dP}{dt} = P^2, \quad P(0) = P_0 \quad \text{where, } P_0 > 0$$

By taking the limit  $\lim_{t\to \frac{1}{P_0}^-} P(t)$ , deduce the appropriateness of the *doomsday* label.

## Solutions

## Section 5: First Order Equations Models and Applications

(1) 
$$q(t) = E_0 C_0 (1 - e^{-t/R_0 C_0}), \quad q \to E_0 C_0 \quad \text{as} \quad t \to \infty.$$

(2) 
$$i(t) = \frac{1}{95}e^{-t} + \frac{94}{95}e^{-20t}$$

(3) 
$$\frac{dA}{dt} + \frac{1}{100}A = 12$$
,  $A(0) = 10$ .  $A(t) = 1200 - 1190e^{-t/100}$ 

(4) 
$$\frac{dA}{dt} + \frac{5}{400 - t}A = 12$$
,  $A(0) = 10$ .  $A(t) = 3(400 - t) - \frac{1190}{400^5}(400 - t)^5$ ,  $0 \le t \le 400$ 

(5) 
$$i(t) = \frac{E_0}{R_0} + \left(i_0 - \frac{E_0}{R_0}\right) e^{-R_0 t/L_0}, \quad \lim_{t \to \infty} i(t) = \frac{E_0}{R_0} + \left(i_0 - \frac{E_0}{R_0}\right) \cdot 0 = \frac{E_0}{R_0}$$

(6) 
$$P(t) = \frac{P_0}{1 - P_0 t}, \quad \lim_{t \to \frac{1}{P_0}^-} P(t) = \infty,$$

Notice that the solution P exibits *blow up* (i.e. tends to infinity) in finite time.