

## Section 11: Linear Mechanical Equations

**Driven Motion:** We can consider the application of an external driving force (with or without damping). Assume a time dependent force  $f(t)$  is applied to the system. The ODE governing displacement becomes

$$m \frac{d^2 x}{dt^2} = -\beta \frac{dx}{dt} - kx + f(t), \quad \beta \geq 0.$$

Divide out  $m$  and let  $F(t) = f(t)/m$  to obtain the nonhomogeneous equation

$$\frac{d^2 x}{dt^2} + 2\lambda \frac{dx}{dt} + \omega^2 x = F(t)$$

# Forced Undamped Motion and Resonance

We considered the case that the forcing was a simple sine (or cosine).

$$x'' + \omega^2 x = F_0 \sin(\gamma t).$$

The complementary solution is

$$x_c = c_1 \cos(\omega t) + c_2 \sin(\omega t),$$

and the particular solution will look like

$$x_p = A \cos(\gamma t) + B \sin(\gamma t) \quad \text{if } \gamma \neq \omega, \text{ or}$$

$$x_p = At \cos(\omega t) + Bt \sin(\omega t) \quad \text{if } \gamma = \omega.$$

# Forced Undamped Motion and Resonance

For  $F(t) = F_0 \sin(\gamma t)$  starting from rest at equilibrium:

$$\text{Case (1): } x'' + \omega^2 x = F_0 \sin(\gamma t), \quad x(0) = 0, \quad x'(0) = 0$$

$$x(t) = \frac{F_0}{\omega^2 - \gamma^2} \left( \sin(\gamma t) - \frac{\gamma}{\omega} \sin(\omega t) \right)$$

**If  $\gamma \approx \omega$ , the amplitude of motion could be rather large!**

## Pure Resonance

Case (2):  $x'' + \omega^2 x = F_0 \sin(\omega t)$ ,  $x(0) = 0$ ,  $x'(0) = 0$

$$x(t) = \frac{F_0}{2\omega^2} \sin(\omega t) - \frac{F_0}{2\omega} t \cos(\omega t)$$

**Note that the amplitude,  $\alpha$ , of the second term is a function of  $t$ :**

$$\alpha(t) = \frac{F_0 t}{2\omega}$$


**which grows without bound!**

► Forced Motion and Resonance Applet

Choose "Elongation diagram" to see a plot of displacement. Try exciter frequencies close to  $\omega$ .

## Section 12: LRC Series Circuits

Potential Drops Across Components:

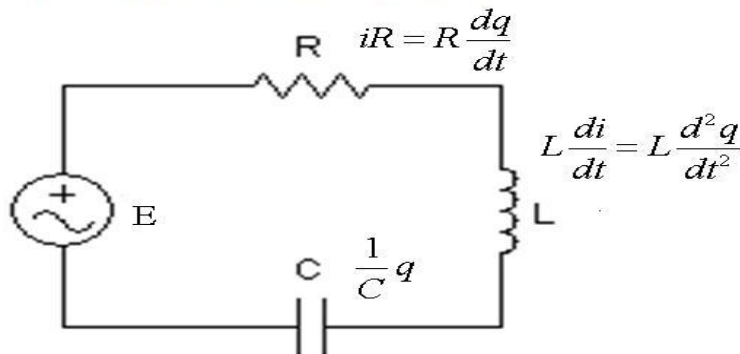

**Figure:** Kirchhoff's Law: The charge  $q$  on the capacitor satisfies  $Lq'' + Rq' + \frac{1}{C}q = E(t)$ .

This is a second order, linear, constant coefficient nonhomogeneous (if  $E \neq 0$ ) equation.

## LRC Series Circuit (Free Electrical Vibrations)

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = 0$$

If the applied force  $E(t) = 0$ , then the **electrical vibrations** of the circuit are said to be **free**. These are categorized as

**overdamped** if

$$R^2 - 4L/C > 0,$$

2 real roots

**critically damped** if

$$R^2 - 4L/C = 0,$$

1 real root

**underdamped** if

$$R^2 - 4L/C < 0.$$

complex roots

# Steady and Transient States

Given a nonzero applied voltage  $E(t)$ , we obtain an IVP with nonhomogeneous ODE for the charge  $q$

$$Lq'' + Rq' + \frac{1}{C}q = E(t), \quad q(0) = q_0, \quad q'(0) = i_0.$$

From our basic theory of linear equations we know that the solution will take the form

$$q(t) = q_c(t) + q_p(t).$$

The function of  $q_c$  is influenced by the initial state ( $q_0$  and  $i_0$ ) and will decay exponentially as  $t \rightarrow \infty$ . Hence  $q_c$  is called the **transient state charge** of the system.

# Steady and Transient States

Given a nonzero applied voltage  $E(t)$ , we obtain an IVP with nonhomogeneous ODE for the charge  $q$

$$Lq'' + Rq' + \frac{1}{C}q = E(t), \quad q(0) = q_0, \quad q'(0) = i_0.$$

From our basic theory of linear equations we know that the solution will take the form

$$q(t) = q_c(t) + q_p(t).$$

The function  $q_p$  is independent of the initial state but depends on the characteristics of the circuit ( $L$ ,  $R$ , and  $C$ ) and the applied voltage  $E$ .  $q_p$  is called the **steady state charge** of the system.

Steady state current  $i_p = \frac{dq_p}{dt}$



## Example

An LRC series circuit has inductance 0.5 h, resistance 10 ohms, and capacitance  $4 \cdot 10^{-3}$  f. Find the steady state current of the system if the applied force is  $E(t) = 5 \cos(10t)$ .

The ODE is

$$Lq'' + Rq' + \frac{1}{C}q = E$$

Here,  $L = \frac{1}{2}$ ,  $R = 10$ ,  $C = 4 \cdot 10^{-3}$

$$\frac{1}{2}q'' + 10q' + \frac{1}{4 \cdot 10^{-3}}q = 5 \cos(10t)$$

We're asked to find Steady State Current,

$i_p = \frac{dq_p}{dt}$ . We'll use undetermined

coefficients to find  $q_p$ .

$$\frac{1}{4 \cdot 10^{-3}} = \frac{10^3}{4} = \frac{1000}{4} = 250$$

In standard form, the ODE is

$$q'' + 20q' + 500q = 10 \cos(10t)$$

Find  $q_c$ : Characteristic eqn

$$m^2 + 20m + 500 = 0$$

$$m^2 + 20m + 100 - 100 + 500 = 0$$

$$(m+10)^2 = -400$$

$$m+10 = \pm 20i \Rightarrow m = -10 \pm 20i$$

$$q_c = c_1 e^{-10t} \cos(20t) + c_2 e^{-10t} \sin(20t)$$

Find  $q_p$ :  $q'' + 20q' + 500q = 10 \cos(10t)$

$$g(t) = 10 \cos(10t)$$

$$q_p = A \cos(10t) + B \sin(10t)$$

This has no like terms in common w/  $q_c$   
so it is correct.

$$q_p' = -10A \sin(10t) + 10B \cos(10t)$$

$$q_p'' = -100A \cos(10t) - 100B \sin(10t)$$

$$q_p'' + 20q_p' + 500q_p = 10 \cos(10t)$$

$$\begin{aligned}
& -100 \underline{A \cos(10t)} - 100 \underline{B \sin(10t)} + 20 \left( -10 \underline{A \sin(10t)} + 10 \underline{B \cos(10t)} \right) \\
& + 500 \left( \underline{A \cos(10t)} + \underline{B \sin(10t)} \right) \\
& = 10 \cos(10t) + 0 \sin(10t)
\end{aligned}$$

$\uparrow$   
 $200$

Collect  $\cos(10t)$  and  $\sin(10t)$

$$\begin{aligned}
& \cos(10t) \left( -100A + 200B + 500A \right) + \sin(10t) \left( -100B - 200A + 500B \right) \\
& = 10 \cos(10t) + 0 \sin(10t)
\end{aligned}$$

$$400A + 200B = 10$$

$$-200A + 400B = 0 \Rightarrow A = 2B$$

$$40A + 20B = 1 \Rightarrow 40(2B) + 20B = 1$$

$$100B = 1$$

$$B = \frac{1}{100} \quad A = \frac{2}{100}$$

The steady state charge is

$$q_p = \frac{1}{50} \cos(10t) + \frac{1}{100} \sin(10t)$$

The steady state current

$$i_p = \frac{dq_p}{dt} = -\frac{10}{50} \sin(10t) + \frac{10}{100} \cos(10t)$$

$$i_p = \frac{1}{10} \cos(10t) - \frac{1}{8} \sin(10t)$$