# October 17 Math 2306 sec. 52 Fall 2022 Section 12: LRC Series Circuits

Potential Drops Across Components:



Figure: Kirchhoff's Law: The charge *q* on the capacitor satisfies  $Lq'' + Rq' + \frac{1}{C}q = E(t)$ .

This is a second order, linear, constant coefficient nonhomogeneous (if  $E \neq 0$ ) equation.

October 14, 2022

1/10

#### LRC Series Circuit (Free Electrical Vibrations)

$$L\frac{d^2q}{dt^2} + R\frac{dq}{dt} + \frac{1}{C}q = 0$$

If the applied force E(t) = 0, then the **electrical vibrations** of the circuit are said to be **free**. These are categorized as

overdamped if $R^2 - 4L/C > 0$ , (2 real roots)critically damped if $R^2 - 4L/C = 0$ , (1 real root)underdamped if $R^2 - 4L/C < 0$ . (complex roots)

## **Steady and Transient States**

Given a nonzero applied voltage E(t), we obtain an IVP with nonhomogeneous ODE for the charge q

$$Lq'' + Rq' + \frac{1}{C}q = E(t), \quad q(0) = q_0, \quad q'(0) = i_0.$$

From our basic theory of linear equations we know that the solution will take the form

$$q(t)=q_c(t)+q_p(t).$$

The function of  $q_c$  is influenced by the initial state ( $q_0$  and  $i_0$ ) and will decay exponentially as  $t \to \infty$ . Hence  $q_c$  is called the **transient state charge** of the system.

### **Steady and Transient States**

Given a nonzero applied voltage E(t), we obtain an IVP with nonhomogeneous ODE for the charge q

$$Lq'' + Rq' + \frac{1}{C}q = E(t), \quad q(0) = q_0, \quad q'(0) = i_0.$$

From our basic theory of linear equations we know that the solution will take the form

$$q(t) = q_c(t) + q_p(t).$$
Sleady state current  $i_p = \frac{d_{g,p}}{dt}$ 

The function  $q_p$  is independent of the initial state but depends on the characteristics of the circuit (*L*, *R*, and *C*) and the applied voltage *E*.  $q_p$  is called the **steady state charge** of the system.

## Example

An LRC series circuit has inductance 0.5 h, resistance 10 ohms, and capacitance  $4 \cdot 10^{-3}$  f. Find the steady state current of the system if the applied force is  $E(t) = 5 \cos(10t)$ .

The ODE is Lg" + Rg" + Cq= E L= 2, R= 10, C= .4.103, E= 5Gs (10+)  $\frac{1}{2}q'' + 10q' + \frac{1}{4.10^{-3}}q = 5 \cos(10t)$ well find go and then ip= gp  $\frac{1}{4.6^{-3}} = \frac{10^3}{4} = \frac{1000}{4} = 250$ イロト 不得 トイヨト イヨト 二日

October 14, 2022 5/10

Stendera form q" + 20q' + 500 g = 10 Cus(10t)  $m_{3} + 50m + 800 = 0$ Find ge? M2+20m+100-100 + 500 = 0  $(m+10)^{2}+400 = 0$  $(m+10)^2 = -400$  $m_{\pm 10} = \pm \sqrt{-400} = \pm 200$ m=-10±200  $q_1 = e^{-i 0 t} C_{os}(z \circ t)$ ,  $q_2 = e^{-i 0 t} S_{in}(z \circ t)$ 

< □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □ > < □

Find 
$$q_{P}$$
:  $q'' + 20q' + 500q = 10 Cos(104)$   
 $q_{I}$  Let's use MUC  
Soo  $q_{P} = A Cos(10t) + B Sim(10t)$   $C_{s,s,m}^{or}$   
 $zo \qquad  $q_{P}'' = -10 A Sim(10t) + 10 B Cos(10t)$   
 $1 \qquad  $q_{I}'' = -100 A Cos(10t) + 100B Sim(10t)$   
 $q_{P}'' + 20q_{P}' + 500q_{P} = 10 Cos(10t) + 0 Sim(10t)$   
 $c_{I}s(10t)(-100A + 200B + 500A) + Sim(10t)(-100B - 200A + 500B)$   
 $cos(10t)(-100A + 200B + 500A) + Sim(10t)(-100B - 200A + 500B)$$$ 

= 10 Gs(10+) + 0 Sin(10+)



October 14, 2022 8/10

The steady state current ip = gy  $i_{p} = \frac{2}{100} (-10) \sin(10t) + \frac{1}{100} (10) \cos(10t)$  $i_{p} = \frac{1}{10} \cos(10t) - \frac{2}{10} \sin(10t)$